

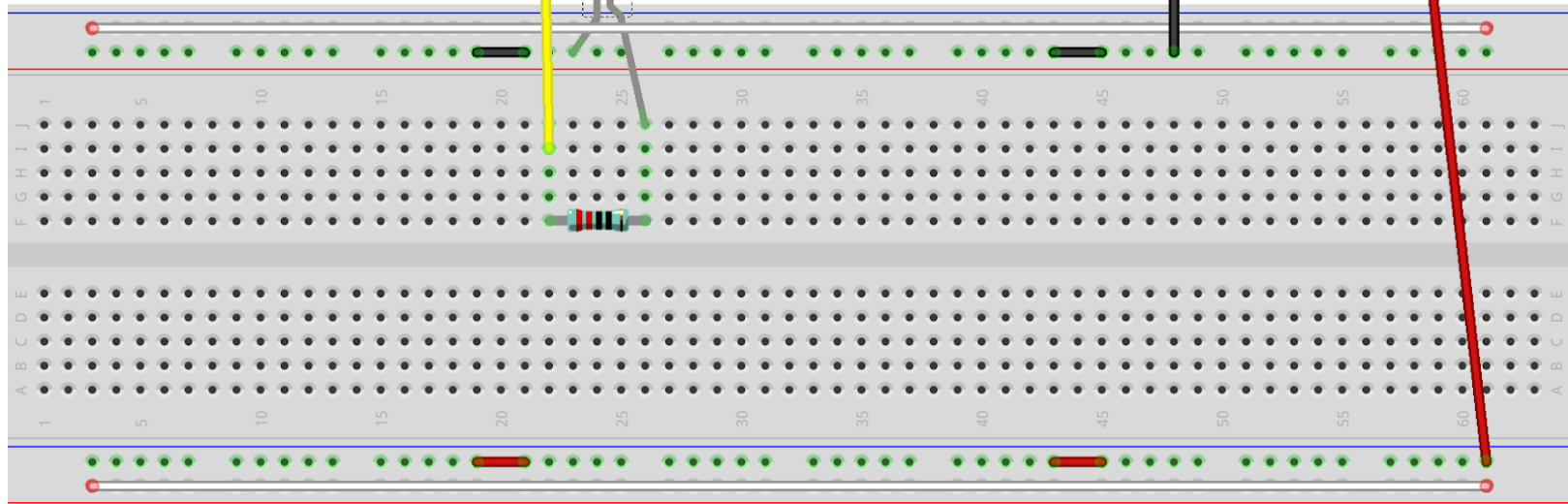


Blink

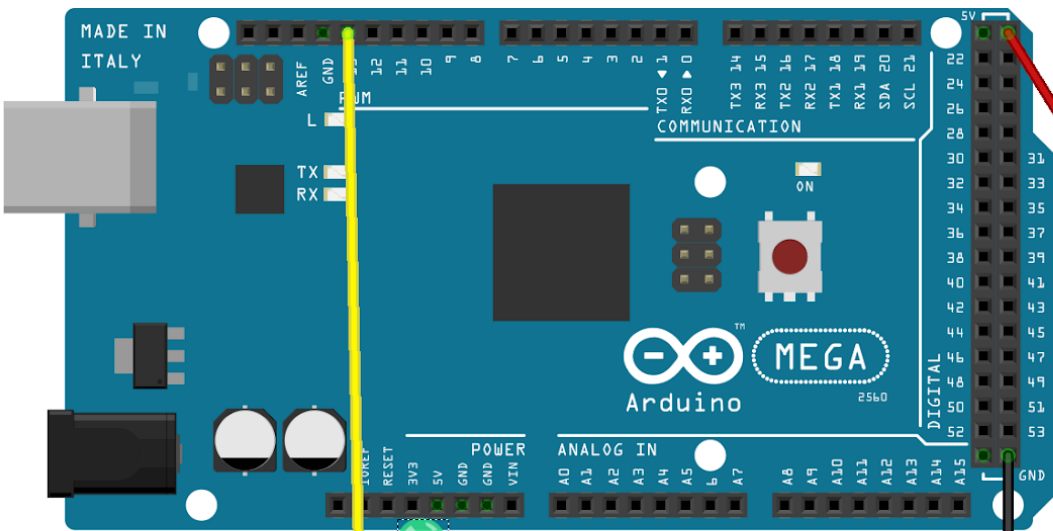


fritzing


Blink and Bump Sensors

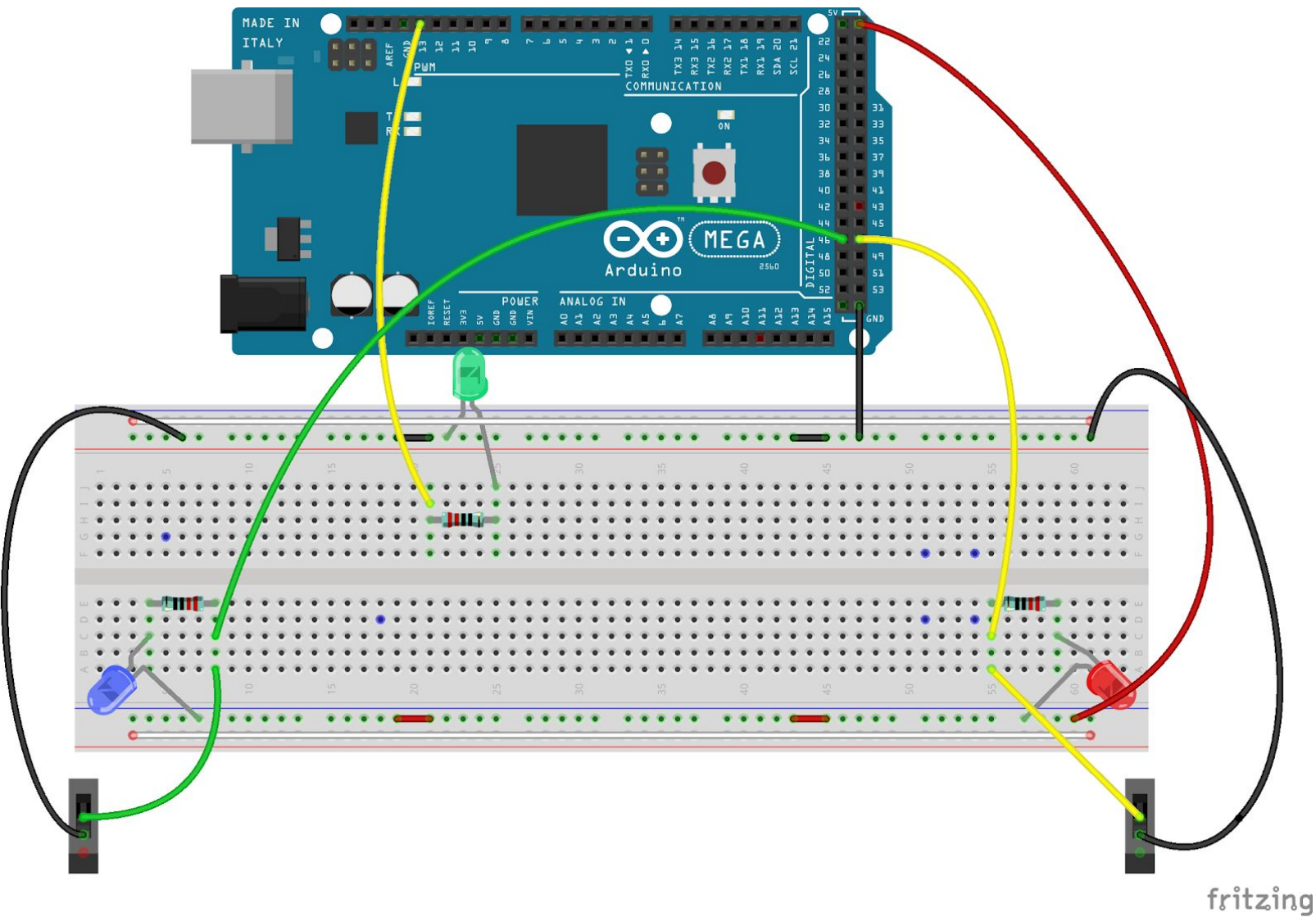

Blink, Bump and Light

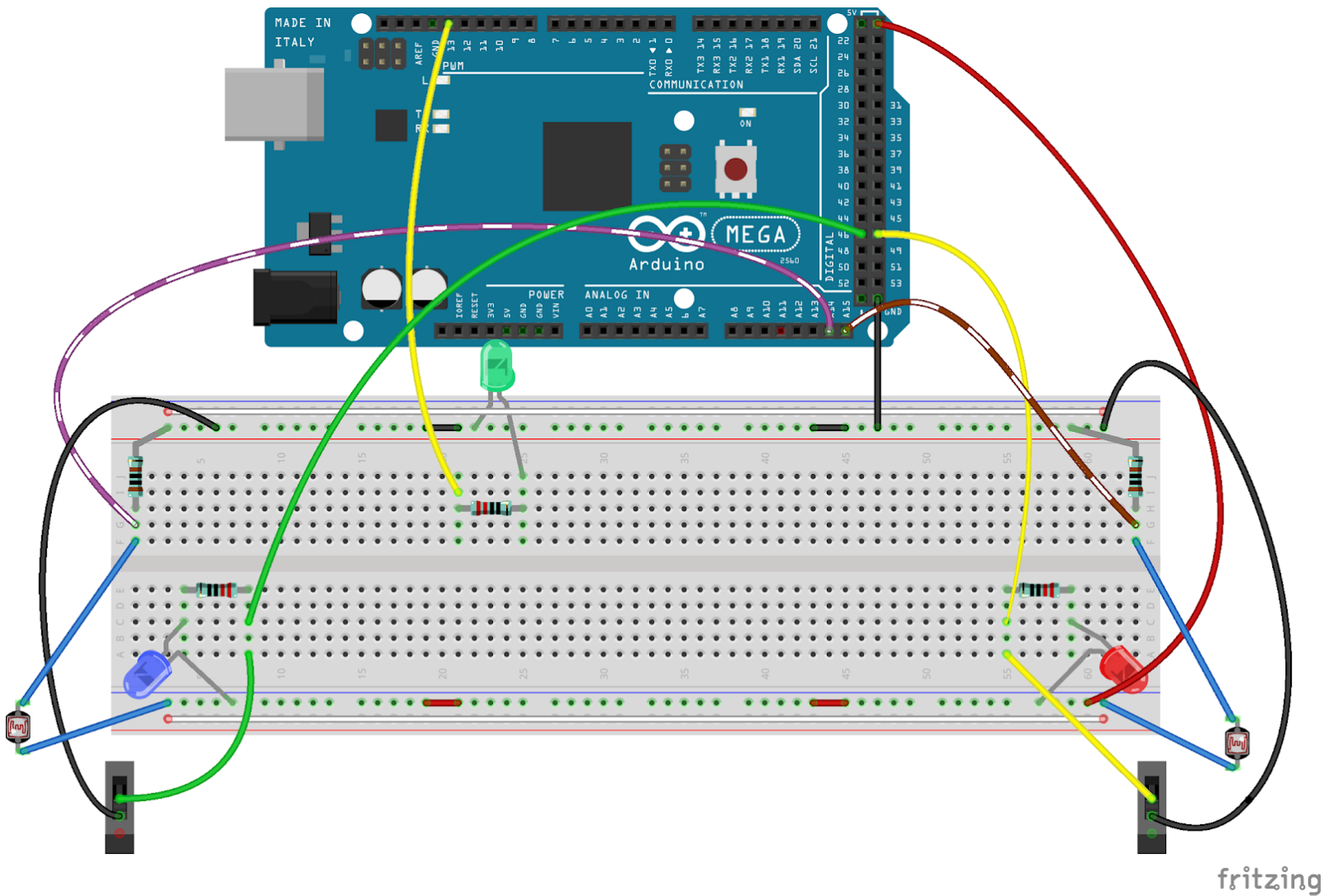

Blink, Bump, Light and Line Sensor

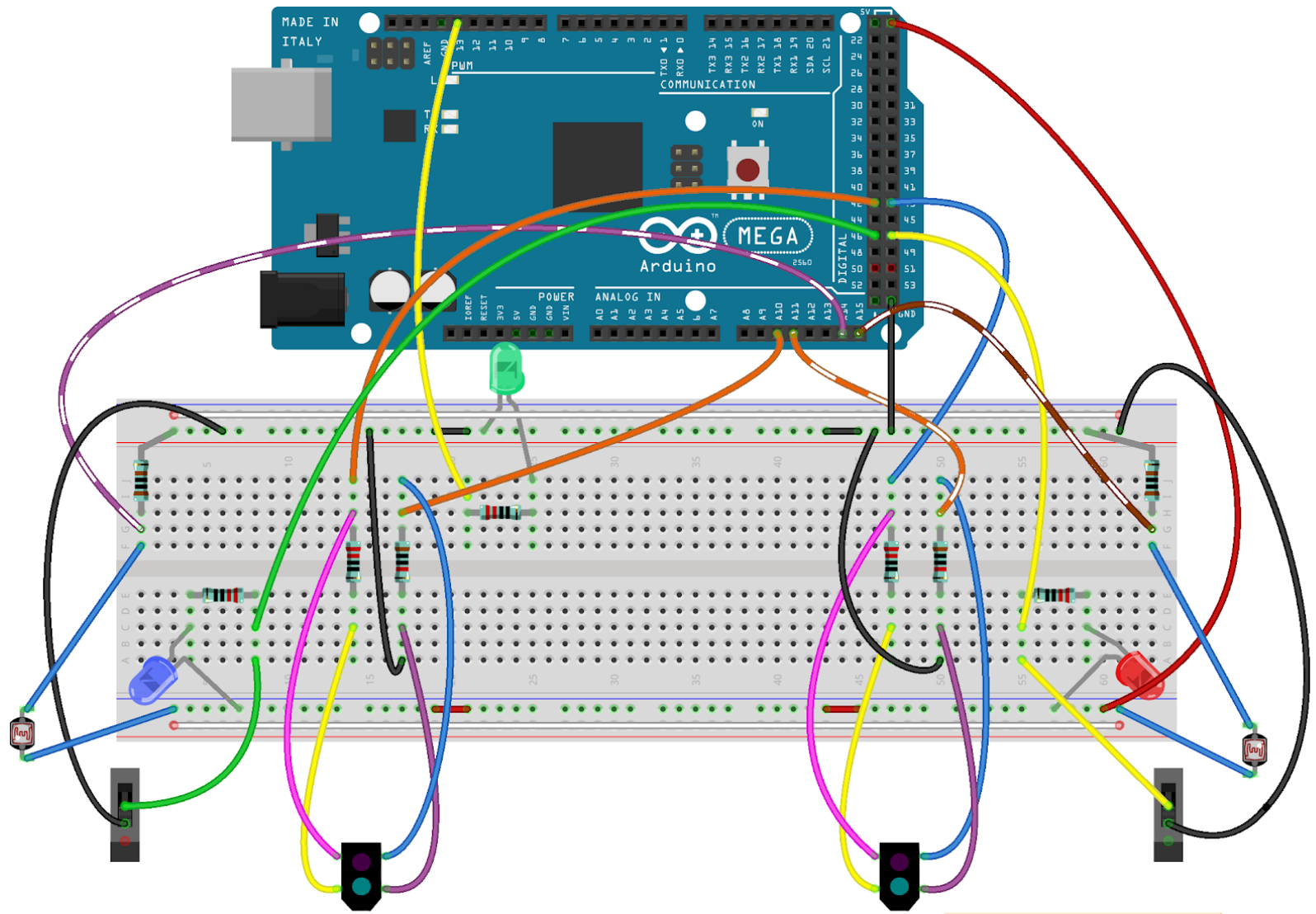

IR Light sensor wiring is shown as if looking down on the back of the sensors, i.e. as they are mounted.

Blink, Bump, Light, Line and Sonic Sensor

